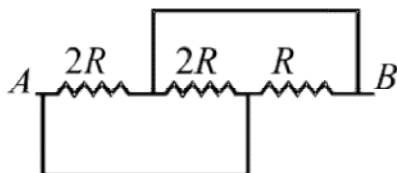


**PHYSICS**


**ELECTRIC CHARGES AND FIELDS,  
ELECTRIC POTENTIAL AND  
CAPACITORS AND CURRENT  
ELECTRICITY**

91. A uniform metallic wire has a resistance of  $18 \Omega$  and is bent into an equilateral triangle. Then, the resistance between any two vertices of the triangle is
- (1)  $12 \Omega$  (2)  $8 \Omega$   
(3)  $2 \Omega$  (4)  $4 \Omega$
92. A steady current flows in a metallic conductor of non-uniform cross-section. The quantity/quantities constant along the length of the conductor is/are
- (1) current, electric field and drift speed  
(2) drift speed only  
(3) current and drift speed  
(4) current only
93. A piece of copper and another of germanium are cooled from room temperature to  $80 \text{ K}$ . The resistance of
- (1) each of them increases  
(2) each of them decreases  
(3) copper increases and germanium decreases  
(4) copper decreases and germanium increases
94. The equivalent resistance between points A and B of the circuit given below is.....




- (1)  $\frac{R}{2}$  (2)  $2R$   
(3)  $5R$  (4)  $3R$

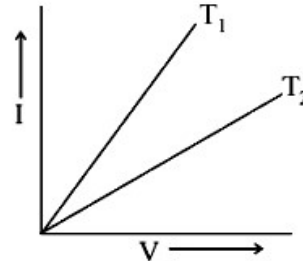
95. The current-voltage graphs for a given metallic wire at two different temperatures  $T_1$  and  $T_2$  are shown in the figure.



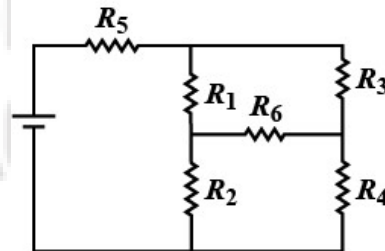- (1)  $T_1 = T_2$   
(2)  $T_1 > T_2$   
(3)  $T_1 < T_2$   
(4)  $T_1 = T_2 = 0$
96. In the given circuit, it is observed that the current  $I$  is independent of the value of the resistance  $R_6$ . Then, the resistance values must satisfy




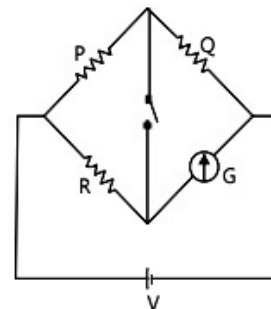- (1)  $R_1 R_2 R_5 = R_3 R_4 R_6$   
(2)  $\frac{1}{R_5} + \frac{1}{R_6} = \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4}$   
(3)  $R_1 R_4 = R_2 R_3$   
(4)  $R_1 R_3 = R_2 R_4$
97. In the circuit shown  $P \neq R$ , the reading of galvanometer is same with switch  $S$  open or closed. Then




- (1)  $I_R = I_G$                       (2)  $I_P = I_G$   
 (3)  $I_Q = I_G$                       (4)  $I_Q = I_R$

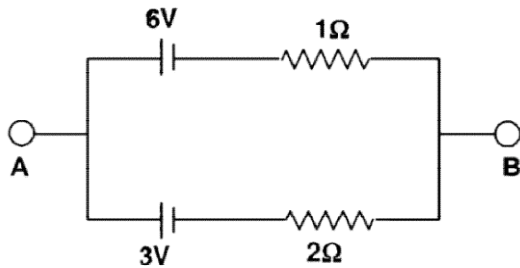98. Two batteries of different emfs and different internal resistances are connected as shown. The voltage across AB in volt is



- (1) 5 V                                  (2) 9 V  
 (3) 2 V                                  (4) 18 V

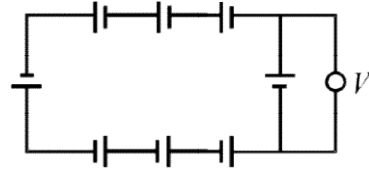99. In the circuit shown below, each battery is 5 V and has an internal resistance of  $0.2 \Omega$



The reading in the ideal voltmeter V is \_\_\_\_\_ V.

- (1) 0 V                                  (2) 40 V  
 (3) 5 V                                  (4) 1 V

100. A cell of internal resistance  $r$  drives current through an external resistance  $R$ . The power delivered by the cell to the external resistance will be maximum when

- (1)  $R = 2r$                               (2)  $R = r$   
 (3)  $R = 0.001r$                       (4)  $R = 1000 r$

