

PHYSICS

111. (1)


Resistance $R = \frac{\Delta V}{\Delta I}$ which is negative in region AB.

112. (3)


$$V_y - V_x = (20 + 5)(0.1) = 2.5 \text{ V}$$

113. (2)

114. (4)

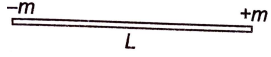
Here, $\frac{E_1 + E_2}{E_1 - E_2} = \frac{5}{10}$ 
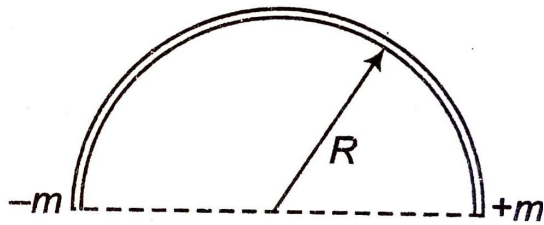
$$\Rightarrow \frac{2E_1}{2E_2} = \frac{50 + 10}{50 - 10} = \frac{60}{40} \Rightarrow \frac{E_1}{E_2} = \frac{3}{2}$$



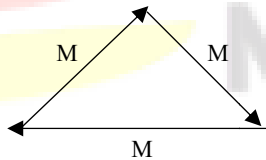115. (2)

Resultant dipole moment of the system = 0



116. (4)

117. (4)

118. (4)

119. (1)

120. (2)