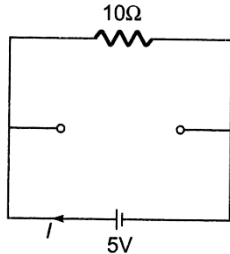


PHYSICS

11. (1)

12. (2)

$$I = \frac{5}{10} = 0.5 \text{ A}$$




13. (2)

Since diode is in forward bias

$$i = \frac{\Delta V}{R} = \frac{4 - (-6)}{1 \times 10^3} = \frac{10}{10^3} = 10^{-2} \text{ A}$$

14. (2)

15. (2)

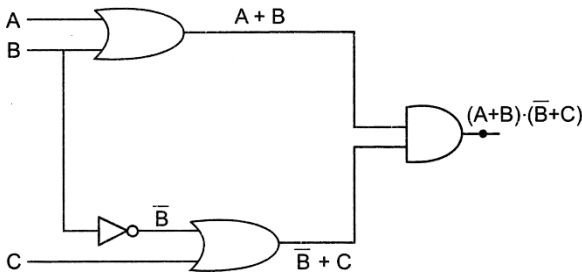

16. (4)

A bulb is essentially a resistance, $R = \frac{V^2}{P}$

where P denotes the power of the bulb.

$$\therefore \text{Resistance of } B_1 (R_1) = \frac{V^2}{100}$$

$$\text{Resistance of } B_2 (R_2) = \frac{V^2}{60}$$

$$\text{Resistance of } B_3 (R_3) = \frac{V^2}{60}$$

$$\therefore I_1 = \text{Current in } B_1 = \frac{250}{(R_1 + R_2)} = \frac{250 \times 300}{8V^2}$$

$$I_2 = \text{Current in } B_2 = \frac{250}{(R_1 + R_2)} = \frac{250 \times 300}{8V^2}$$

$$I_3 = \text{Current in } B_3 = \frac{250}{R_3} = \frac{250 \times 60}{V^2}$$

$$\therefore W_1 = \text{output power of } B_1 = I_1^2 R_1$$

$$\therefore W_1 = \left(\frac{250 \times 300}{8V^2} \right)^2 \times \frac{V^2}{100}$$

$$W_2 = I_2^2 R_2 \text{ or } W_2 = \left(\frac{250 \times 300}{8V^2} \right)^2 \times \frac{V^2}{60}$$

$$W_3 = I_3^2 R_3 \text{ or } W_3 = \left(\frac{250 \times 60}{V^2} \right)^2 \times \frac{V^2}{60}$$

$$\therefore W_1 : W_2 : W_3 = 15 : 25 : 64$$

$$\text{or } W_1 < W_2 < W_3$$

17. (1)


Consider upper segment above PQ.

It is a balanced Wheatstone bridge.

The central resistance 2R becomes ineffective.

Similarly in the lower segment, the central resistance 2R becomes ineffective.

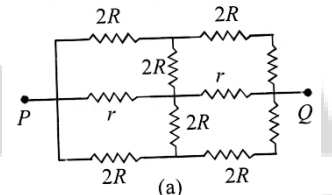
The equivalent circuit is shown in the figure.



$$\therefore \frac{1}{R_{PQ}} = \frac{1}{4R} + \frac{1}{2r} + \frac{1}{4R}$$

$$\text{or } \frac{1}{R_{PQ}} = \frac{r + 2R + r}{4Rr}$$
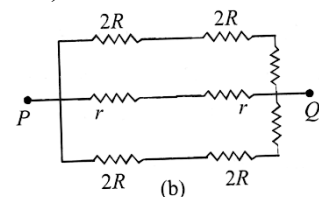
$$R_{PQ} = \frac{4Rr}{2(R+r)} = \frac{2Rr}{R+r}$$



$$\therefore R_{PQ} = \frac{2Rr}{R+r}$$

18. (4)

Copper is a metal. Its resistance decreases when temperature falls.

Germanium is a semiconductor. Its resistance increases when temperature falls.

19. (4)

R_0 = Resistance at 0°C

$$1 \Omega = R_0 (1 + 27\alpha) \text{ and } 2 \Omega = R_0 (1 + T\alpha)$$

$$\frac{2}{1} = \frac{1 + T\alpha}{1 + 27\alpha} \text{ or } T = 854^\circ\text{C} = 127 \text{ K}$$

20. (1)

Current flowing through copper rod is given by

$$I = neAv_d = \rho Av_d \quad (\because \rho = ne)$$

$$v_d = \frac{I}{\rho A}$$

Time taken by charges to travel distance d,

$$t = \frac{d}{v_d} = \frac{d}{\left(\frac{I}{\rho A}\right)} = \frac{\rho Ad}{I}$$

**PARISHRAMA
NEET ACADEMY**