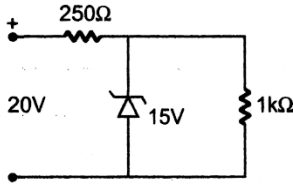



PHYSICS

11. A Zener diode, having breakdown voltage equal to 15 used in a voltage regulator circuit shown in the figure current through the diode is




- (1) 5 mA
- (2) 10 mA
- (3) 15 mA
- (4) 20 mA

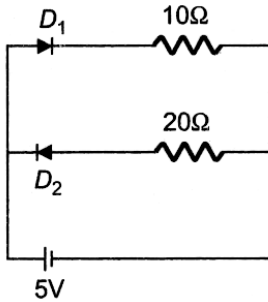12. Two ideal diodes are connected to a battery as shown in circuit. The current supplied by the battery is




- (1) 0.25 A
- (2) 0.5 A
- (3) 0.75 A
- (4) zero

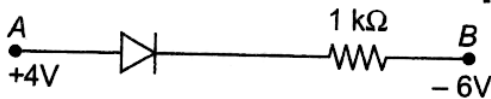13. Consider the junction diode as ideal. The value of current flowing through AB is




- (1) 0 A
- (2) 10^{-2} A
- (3) 10^{-1} A
- (4) 10^{-3} A

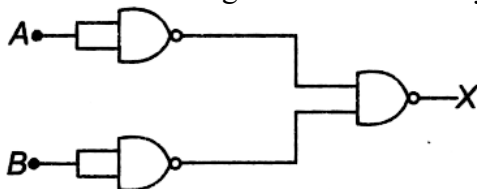14. The combination of gates shown below yields




- (1) NAND gate
- (2) OR gate
- (3) NOT gate
- (4) XOR gate

15. Find out value of Y

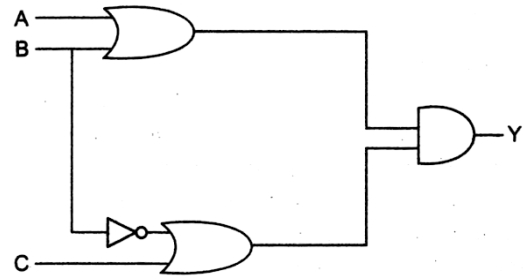


- (1) $(\bar{A} + B) \cdot (\bar{B} + C)$
- (2) $(A + B) \cdot (\bar{B} + C)$
- (3) $(A + \bar{B}) \cdot (B + \bar{C})$
- (4) $(\bar{A} + B) \cdot (\bar{B} + \bar{C})$

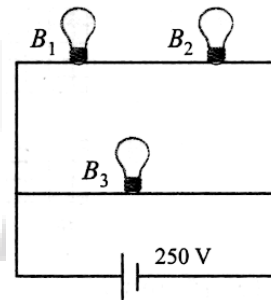16. A 100 W bulb B_1 and two 60 W bulbs B_2 and B_3 , are connected to a 250 V source, as shown in figure. Now W_1, W_2 and W_3 are the output powers of the bulbs B_1, B_2 and B_3 , respectively. Then



- (1) $W_1 > W_2 = W_3$
- (2) $W_1 > W_2 > W_3$
- (3) $W_1 < W_2 = W_3$
- (4) $W_1 < W_2 < W_3$

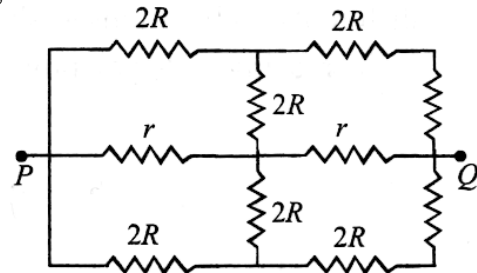17. The effective resistance between points P and Q of the electrical circuit shown in the figure is



- (1) $\frac{2Rr}{R+r}$
- (2) $\frac{8R(R+r)}{3R+r}$
- (3) $2r + 4R$
- (4) $\frac{5R}{2} + 2r$

18. A piece of copper and another of germanium are cooled from room temperature to 80 K. The resistance of
- (1) each of them increases
 - (2) each of them decreases
 - (3) copper increases and germanium decreases
 - (4) copper decreases and germanium increases.
19. The temperature coefficient of resistance of a wire is 0.00125 per °C. At 300 K, its resistance is 1 Ω. This resistance of the wire will be 2 Ω at
- (1) 1154 K
 - (2) 1100 K
 - (3) 1400 K
 - (4) 1127 K
20. A copper rod of cross-sectional area A carries a uniform current I through it. At temperature T, if the volume charge density of the rod is ρ, how long will the charges take to travel a distance d?
- (1) $\frac{\rho d A}{I}$
 - (2) $\frac{\rho d A}{IT}$
 - (3) $\frac{2\rho d A}{I}$
 - (4) $\frac{2\pi d A}{IT}$