

# PHYSICS

21. (4) Resistance of the bulb

$$(R) = \frac{V^2}{P} = \frac{(220)^2}{100} = 484 \Omega$$

$$\text{Power across 110 volt} = \frac{(110)^2}{484}$$

$$\therefore \text{Power} = \frac{110 \times 110}{484} = 25 \text{ W}$$

22. (2) The internal resistance of a cell is given by

$$r = R \left( \frac{l_1}{l_2} - 1 \right) = R \left( \frac{l_1 - l_2}{l_2} \right)$$

$$\therefore r = 2 \left[ \frac{240 - 120}{120} \right] = 2 \Omega$$

23. (4) Resistance of the conducting wire,

$$R_1 = \frac{\rho l}{A}$$

When length of the wire is doubled, its length becomes  $l' = 2l$

$$\text{New area of cross section, } A' = \frac{A}{2}$$

$$R_2 = \frac{\rho \times (2l)}{\left(\frac{A}{2}\right)} = 4 \frac{\rho l}{A}$$

From the ohm's law,  $V = IR$

$$\therefore \text{Current, } I = \frac{V}{R_2} = \frac{V}{\left(\frac{4\rho l}{A}\right)} \Rightarrow I = \frac{1}{4} \frac{VA}{\rho l}$$

24. (4) Number 2 is associated with the red colour.

This colour is replaced by green.

Since, colour code figure for green is 5.


Therefore, new resistance = 500  $\Omega$

25. (1) Using,  $I = neAv_d$

$$\therefore \text{Drift speed, } v_d = \frac{1}{neA}$$

$$= \frac{1.5}{9 \times 10^{28} \times 1.6 \times 10^{-19} \times 5 \times 10^{-6}} = 0.02 \text{ mms}^{-1}$$

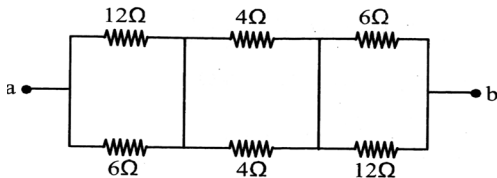26. (1) When switch  $S_1$  and  $S_2$  are closed.



$$\frac{1}{R_1} = \frac{1}{12} + \frac{1}{6} = \frac{1+2}{12} = \frac{1}{4} \therefore R_1 = 4 \Omega$$

$$\frac{1}{R_2} = \frac{1}{4} + \frac{1}{4} = \frac{1+1}{4} \therefore R_2 = \frac{4}{2} = 2 \Omega$$

$$\frac{1}{R_3} = \frac{1}{6} + \frac{1}{12} = \frac{2+1}{12} \therefore R_3 = \frac{12}{3} = 4 \Omega$$

$$\therefore R_{ab} = R_1 + R_2 + R_3 = 4 + 2 + 4 = 10 \Omega$$


$$27. (4) i = \left( \frac{\epsilon}{R+r} \right)$$

Power delivered to R

$$P = i^2 R = \left( \frac{\epsilon}{R+r} \right)^2 R$$

$$P \text{ to be maximum, } \frac{dP}{dR} = 0$$
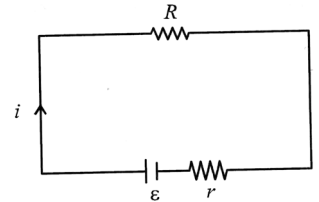
$$\text{or } \frac{d}{dR} \left[ \left( \frac{\epsilon}{R+r} \right)^2 R \right] = 0 \text{ or } R = r$$



28. (2)

Given,  $E_1 = 1 \text{ V}$ ,  $E_2 = 2 \text{ V}$ ,  $E_3 = 3 \text{ V}$ ,  
 $r_1 = 1 \Omega$ ,  $r_2 = 1 \Omega$  and  $r_3 = 1 \Omega$

$$V_{AB} = V_{CD} = \frac{\frac{E_1}{r_1} + \frac{E_2}{r_2} + \frac{E_3}{r_3}}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3}} = \frac{1 + 2 + 3}{\frac{1}{1} + \frac{1}{1} + \frac{1}{1}} = \frac{6}{3} = 2 \text{ V}$$

29. (1)

$$\text{As } R = \frac{V^2}{P}, \text{ so } R_1 = \frac{220^2}{25} \text{ and } R_2 = \frac{220^2}{100}$$

$$\text{Current, } i = \frac{220}{R_1 + R_2}$$

$$P_1 = i^2 R_1 = \frac{220^2}{\left( \frac{220^2}{25} + \frac{220^2}{100} \right)} \times \frac{220^2}{25} = 16 \text{ W}$$

$$\text{Similarly, } P_2 = i^2 R_2 = 4 \text{ W}$$

30. (2)

As Zener diode is heavily doped p-n diode so it has narrow depletion layer.