


# PHYSICS

31. LED is constructed from Ga-As-P semiconducting material. The energy gap of this LED is 1.9 eV. Calculate the wavelength of light emitted and its colour.

[ $h = 6.63 \times 10^{-34} \text{ J s}$  and  $c = 3 \times 10^8 \text{ m s}^{-1}$ ]

- (1) 654 nm and red colour
- (2) 1046 nm and blue colour
- (3) 1046 nm and red colour
- (4) 654 nm and orange colour

32. The current  $i$  in the network is


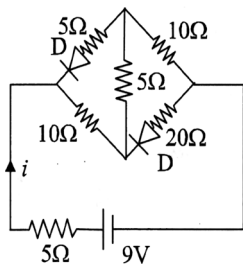


- (1) 0.2 A
- (2) 0.6 A
- (3) 0.3 A
- (4) 0 A

33. Mobility of electrons in a semiconductor is defined as the ratio of their drift velocity to the applied electric field. If, for an n-type semiconductor, the density of electrons is  $10^{19} \text{ m}^{-3}$  and their mobility is  $1.6 \text{ m}^2 \text{ (vs)}$  then the resistivity of the semiconductor (since it is an n-type semiconductor contribution of holes is ignored) is close to

- (1) 2 Ωm
- (2) 4 Ωm
- (3) 0.4 Ωm
- (4) 0.2 Ωm

34. The I-V characteristic of an LED is

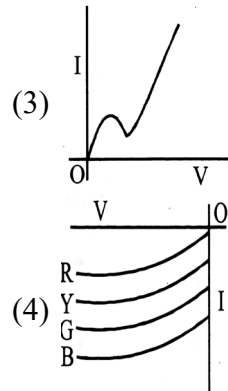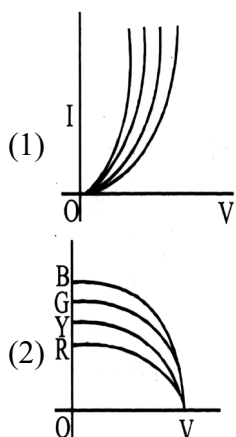


35. Carbon, silicon and germanium have four valence electrons each. At room temperature which one of the following statements is most appropriate?

- (1) The number of free electrons for conduction is significant only in Si and Ge but small in C
- (2) The number of free conduction electrons in significant in C but small in Si and Ge.
- (3) The number of free conduction electrons is negligibly small in all the three
- (4) The number of free electrons for conduction is significant in all the three


36. Identify the logic operation carried out by the given circuit.

- (1) OR
- (2) AND
- (3) NOR
- (4) NAND


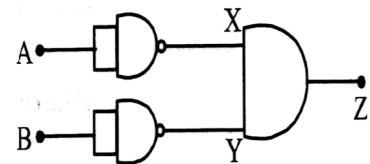


37. The logic gate equivalent to the given circuit is


- (1) NAND
- (2) OR
- (3) NOR
- (4) AND

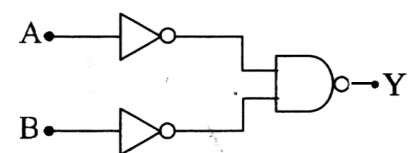

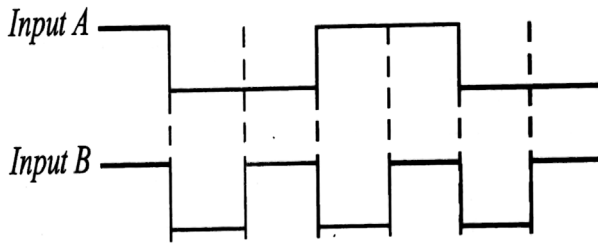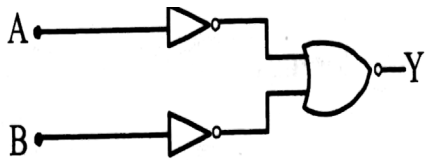38. The logic circuit shown has the input waveforms A and B as shown. Pick out the correct output waveform.




Output is

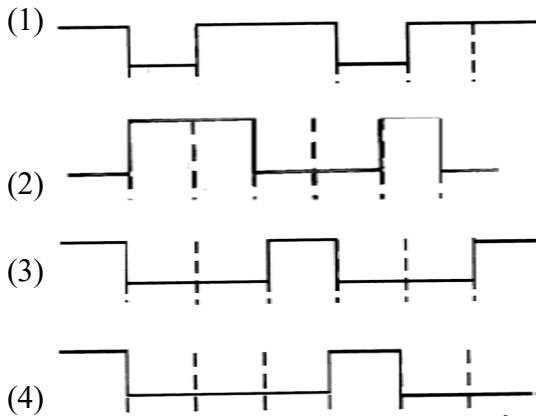


39. In the circuit below, A and B represent two inputs and C represents the output.

The circuit represents

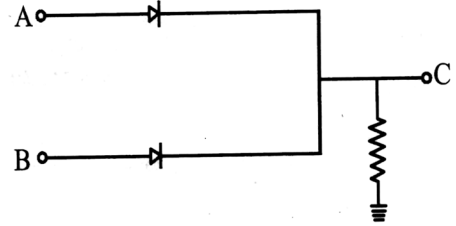

- (1) NOR gate
- (2) AND gate
- (3) NAND gate
- (4) OR gate

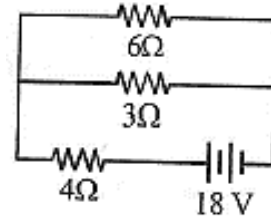40. The total power dissipated in watts in the circuit shown here is



- (1) 40
- (2) 54
- (3) 4
- (4) 16