

PHYSICS

Section A

1. (1)

$$R = \frac{\rho l}{A} \Rightarrow R = \left(\frac{m}{ne^2 \tau} \right) \frac{l}{A}$$

2. (4)

White-Brown-Red

$$R = 91 \times 10^2 \pm 10\% \Rightarrow R = 9.1 \times 10^3 \pm 10\%$$

3. (2)

$$V_d = \frac{i}{neA} \Rightarrow V = \frac{i}{ne(\pi r^2)}$$

$$V' = \frac{2i}{ne\pi(2r)^2} = \frac{2}{4} \left(\frac{i}{ne\pi r^2} \right)$$

$$V' = \frac{1}{2} V \Rightarrow V' = \frac{V}{2}$$

4. (1)

$$R = \frac{\rho l}{A} = \frac{l}{d^2}$$


5. (3)

$$i = \frac{V}{R_e}$$

$$i = \frac{2}{60 \times 30} = \frac{2(90)}{1800} \Rightarrow i = \frac{1}{10} A$$

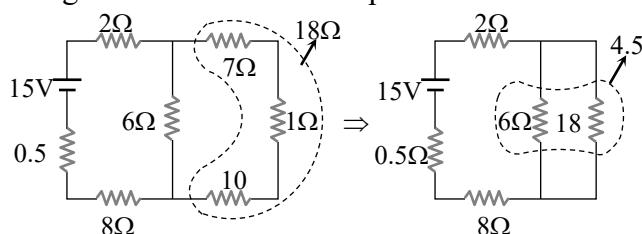6. (1)

The given circuit can be simplified as follows



On further solving equivalent resistance
 $R = 15\Omega$

Hence, current from the battery $i = \frac{15}{15} = 1A$

7. (3)

$$R_{\max} = nR \text{ and } R_{\min} = R/n \Rightarrow \frac{R_{\max}}{R_{\min}} = n^2$$

8. (2)

$$R_{eq} = R_1 + R_2 \Rightarrow \frac{\rho_{eff.2l}}{A} = \frac{\rho_1 l}{A} + \frac{\rho_2 l}{A}$$

$$\Rightarrow \rho_{eff.} = \frac{\rho_1 + \rho_2}{2}$$

9. (2)

$$\text{Let the current in the circuit} = i = \frac{V}{R}$$

$$\text{Across the cell, } E = V + ir$$

$$\Rightarrow r = \frac{E - V}{i} = \frac{E - V}{V/R} = \left(\frac{E - V}{V} \right) R$$

10. (1)

According to Kirchhoff's first law

$$\text{At junction A, } i_{AB} = 2 + 2 = 4A$$

$$\text{At junction B, } i_{BC} = 4 - 1 = 3A$$

