

PHYSICS


Section A

1. If n, e, τ and m respectively represent the density, charge relaxation time and mass of the electron, then the resistance of a wire of length l and area of cross-section A will be

- (1) $\frac{ml}{ne^2\tau A}$ (2) $\frac{m\tau^2 A}{ne^2 l}$
 (3) $\frac{ne^2\tau A}{2ml}$ (4) $\frac{ne^2 A}{2m\tau l}$

2. In the figure a carbon resistor has bands of different colours on its body as mentioned in the figure. The value of the resistance is

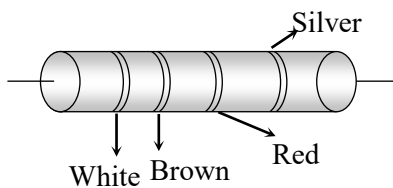- (1) 2.2 k Ω
 (2) 3.3 k Ω
 (3) 5.6 k Ω
 (4) 9.1 k Ω



3. The drift velocity of free electrons in a conductor is ' v ' when a current ' i ' is flowing in it. If both the radius and current are doubled, then drift velocity will be


- (1) v
 (2) $\frac{v}{2}$
 (3) $\frac{v}{4}$
 (4) $\frac{v}{8}$

4. The following four wires are made of the same material and are at the same temperature. Which one of them has highest electrical resistance

- (1) Length = 50 cm, diameter = 0.5 mm
 (2) Length = 100 cm, diameter = 1 mm
 (3) Length = 200 cm, diameter = 2 mm
 (4) Length = 300 cm, diameter = 3 mm


5. The current in the adjoining circuit will be

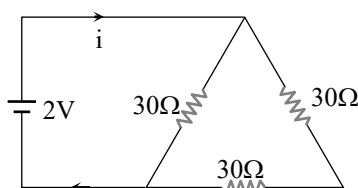- (1) $\frac{1}{45}$ ampere
 (2) $\frac{1}{15}$ ampere
 (3) $\frac{1}{10}$ ampere
 (4) $\frac{1}{5}$ ampere



6. The current from the battery in circuit diagram shown is

- (1) 1 A
 (2) 2 A
 (3) 1.5 A
 (4) 3 A

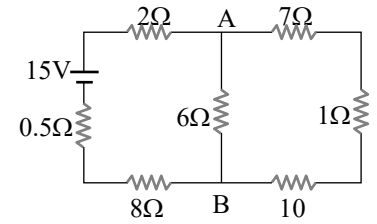

7. n equal resistors are first connected in series and then connected in parallel. What is the ratio of the maximum to the minimum resistance

- (1) n (2) $\frac{1}{n^2}$
 (3) n^2 (4) $\frac{1}{n}$

8. Two wires of the same dimensions but resistivities ρ_1 and ρ_2 are connected in series.

The equivalent resistivity of the combination is

- (1) $\rho_1 + \rho_2$ (2) $\frac{\rho_1 + \rho_2}{2}$
 (3) $\sqrt{\rho_1 \rho_2}$ (4) $2(\rho_1 + \rho_2)$

9. A cell of e.m.f. E is connected with an external resistance R , then p.d. across cell is V . The internal resistance of cell will be

- (1) $\frac{(E - V)R}{E}$ (2) $\frac{(E - V)R}{V}$
 (3) $\frac{(V - E)R}{V}$ (4) $\frac{(V - E)R}{E}$

10. The figure below shows currents in a part of electric circuit. The current i is

- (1) 1.7 amp
 (2) 3.7 amp
 (3) 1.3 amp
 (4) 1 amp

