

11.  $n$  identical cells each of e.m.f.  $E$  and internal resistance  $r$  are connected in series. An external resistance  $R$  is connected in series to this combination. The current through  $R$  is

- (1)  $\frac{nE}{R + nr}$                       (2)  $\frac{nE}{nR + r}$   
 (3)  $\frac{E}{R + nr}$                       (4)  $\frac{nE}{R + r}$

12. When a resistance of 2 ohm is connected across the terminals of a cell, the current is 0.5 A. When the resistance is increased to 5 ohm, the current is 0.25 A. The e.m.f. of the cell is

- (1) 1.0 V  
 (2) 1.5 V  
 (3) 2.0 V  
 (4) 2.5 V

13. In a potentiometer experiment the balancing with a cell is at length 240 cm. On shunting the cell with a resistance of 2  $\Omega$ , the balancing length becomes 120 cm. The internal resistance of the cell is

- (1) 4  $\Omega$   
 (2) 2  $\Omega$   
 (3) 1  $\Omega$   
 (4) 0.5  $\Omega$

14. A cell of emf 6 V and resistance 0.5 ohm is short circuited. The current in the cell is

- (1) 3 amp                      (2) 12 amp  
 (3) 24 amp                      (4) 6 amp

15. In an experiment of meter bridge, a null point is obtained at the centre of the bridge wire. When a resistance of 10 ohm is connected in one gap, the value of resistance in other gap is

- (1) 10  $\Omega$                       (2) 5  $\Omega$   
 (3)  $\frac{1}{5} \Omega$                       (4) 500  $\Omega$

16. If in the experiment of Wheatstone's bridge, the positions of cells and galvanometer are interchanged, then balance points will

- (1) Change  
 (2) Remain unchanged  
 (3) Depend on the internal resistance of cell and resistance of galvanometer  
 (4) None of these

17. In a potentiometer experiment two cells of e.m.f.  $E_1$  and  $E_2$  are used in series and in conjunction and the balancing length is found to be 58 cm of the wire. If the polarity of  $E_2$  is reversed, then the balancing length becomes 29 cm. The ratio  $\frac{E_1}{E_2}$  of the e.m.f. of the two

cells is

- (1) 1 : 1                      (2) 2 : 1  
 (3) 3 : 1                      (4) 4 : 1


18. A uniform metallic wire has a resistance of 18  $\Omega$  and is bent into an equilateral triangle. Then, the resistance between any two vertices of the triangle is

- (1) 12  $\Omega$   
 (2) 8  $\Omega$   
 (3) 2  $\Omega$   
 (4) 4  $\Omega$

19. A steady current flows in a metallic conductor of non-uniform cross-section. The quantity/quantities constant along the length of the conductor is/are

- (1) current, electric field and drift speed  
 (2) drift speed only  
 (3) current and drift speed  
 (4) current only

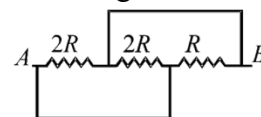20. The equivalent resistance between points A and B of the circuit given below is.....



- (1)  $\frac{R}{2}$                       (2) 2R  
 (3) 5R                      (4) 3R