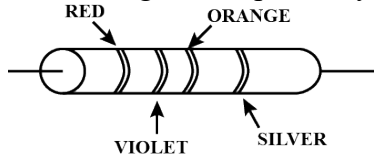


21. A resistance is shown in the figure. Its value and tolerance are given respectively by



- (1) 270Ω , 5%
- (2) $27 \text{ k}\Omega$, 20%
- (3) $27 \text{ k}\Omega$, 10%
- (4) $270 \text{ k}\Omega$, 10%


22. Which of the following statements is false?

- (1) In a balanced Wheatstone bridge, if the cell and the galvanometer are exchanged, the null point is disturbed
- (2) Mobility independent on electric field
- (3) Kirchhoff's second law represents energy conservation
- (4) Wheatstone bridge is the most sensitive when all the four resistances are of the same order of magnitude

23. Dimension of electrical resistance is


- (1) $[\text{ML}^2\text{T}^{-3}\text{A}^{-1}]$
- (2) $[\text{ML}^2\text{T}^{-3}\text{A}^{-2}]$
- (3) $[\text{ML}^3\text{T}^{-3}\text{A}^{-2}]$
- (4) $[\text{ML}^2\text{T}^{-3}\text{A}^{-1}]$

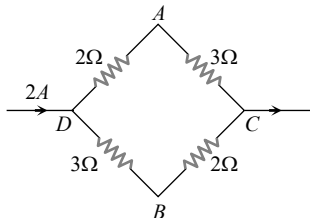24. A current of 2 A flows in a system of conductors as shown. The potential difference ($V_A - V_B$) will be



- (1) $+2\text{ V}$
- (2) $+1\text{ V}$
- (3) -1 V
- (4) -2 V

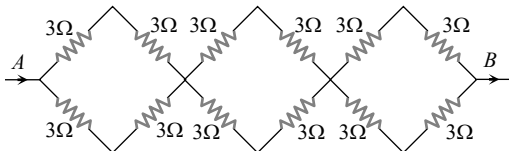25. In the network of resistors shown in the adjoining figure, the equivalent resistance between A and B is




- (1) 54 ohm
- (2) 18 ohm
- (3) 36 ohm
- (4) 9 ohm

26. Kirchhoff's first law i.e. $\Sigma i = 0$ at a junction is based on the law of conservation of

- (1) Charge
- (2) Energy
- (3) Momentum
- (4) Angular momentum

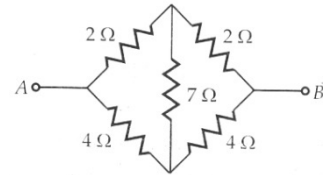27. The equivalent resistance between A and B of the circuit is



- (1) $\frac{13}{12} \Omega$
- (2) $\frac{8}{3} \Omega$
- (3) 8Ω
- (4) $\frac{4}{3} \Omega$

28. Resistance in the two gaps of a meter bridge are 10 ohm and 30 ohm respectively. If the resistances are interchanged the balance point shifts by

- (1) 33.3 cm
- (2) 66.67 cm
- (3) 25 cm
- (4) 50 cm

29. A potentiometer wire is supplied a constant voltage is 3 V. A cell of emf 1.08 V is balanced by the voltage drop across 216 cm of the wire. Find the total length of the potentiometer wire

- (1) 300 cm
- (2) 400 cm
- (3) 600 cm
- (4) 500 cm

30. When current flows through a conductor, then the order of drift velocity of electrons will be

- (1) 10^{10} m / sec
- (2) 10^{-2} cm / sec
- (3) 10^4 cm / sec
- (4) 10^{-1} cm / sec