

41. (1)

(i)  $\rightarrow 3R$

(ii)  $\rightarrow \frac{2R}{3}$

(iii)  $\rightarrow \frac{R}{3}$

(iv)  $\rightarrow \frac{3R}{2}$

42. (4)

$$R \propto \frac{l^2}{m} \Rightarrow R_1 : R_2 : R_3 = \frac{l_1^2}{m_1} : \frac{l_2^2}{m_2} : \frac{l_3^2}{m_3}$$

$$\Rightarrow R_1 : R_2 : R_3 = \frac{9}{1} : \frac{4}{2} : \frac{1}{3} = 27 : 6 : 1$$

43. (2)

The fourth term arm has resistance  $S$  and  $6 \Omega$  in parallel with equivalent resistance  $= \frac{6S}{6+S} \Omega$

For the balanced Wheatstone bridge,

$$\frac{P}{Q} = \frac{R}{\frac{6S}{6+S}} \text{ or } \frac{2}{2} = \frac{2(6+S)}{6S}$$

$$\text{or } 3S = 6 + S \text{ or } S = 3\Omega$$

44. (1)

In the series circuit, same current flows through each bulb. But the  $25 \text{ W}$  bulb has a higher resistance ( $R = V^2/P$ ). It produces more heat per second ( $P = I^2R$ ) and hence glows brighter than  $100 \text{ W}$  bulb

45. (4)

$$(4+r)i = 2.2 \quad \dots\dots(i)$$

$$\text{and } 4i = 2 \Rightarrow i = \frac{1}{2}$$

Putting the value of  $i$  in (i), we get  $r = 0.4 \text{ ohm}$ .

46. (2)

Here  $l = 10 \text{ cm}$ ,  $R = 18 \Omega$ ,  $\varepsilon = 5 \text{ V}$ ,  $r = 2 \Omega$

Current through the potentiometer wire,

$$I = \frac{\varepsilon}{R+r} = \frac{5}{18+2} = \frac{5}{20} = \frac{1}{4} \text{ A}$$

$$\therefore \text{Potential gradient} = \frac{IR}{l} = \frac{1}{4} \times \frac{18}{10} = 0.45 \text{ Vm}^{-1}$$

47. (2)

$$\text{In first case, } \frac{R}{S} = \frac{60}{40} = \frac{3}{2} \quad \dots(i)$$

$$\text{In second case, } \frac{R}{S+5} = \frac{50}{50} \quad \dots(ii)$$

$$\text{On dividing (i) by (ii), } \frac{S+5}{S} = \frac{3}{2}$$

$$\text{or } 2S + 10 = 3S$$

$$\text{or } S = 10 \Omega$$

$$\text{and } R = \frac{3}{2}S = \frac{3}{2} \times 10 = 15\Omega$$

48. (4)

$$r = R \left( \frac{\varepsilon - V}{V} \right) = 14 \left( \frac{1.5 - 1.4}{1.4} \right) = 1\Omega$$

49. (1)

$$\frac{100}{100R} = \frac{200}{40}$$


$$\frac{100R}{100+R} = 20$$

$$\therefore R = 25 \Omega$$

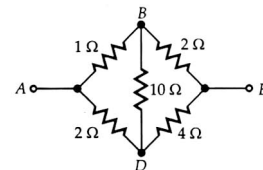50. (1)

$$\text{As } \frac{1}{2} = \frac{2}{4}$$

The above circuit can be written as, the resistance of  $10 \Omega$  is



We have  $(1 \Omega + 2 \Omega)$  and  $(2\Omega + 4\Omega)$  combinations in parallel

$$\therefore R = \frac{3 \times 6}{3+6} = 2\Omega$$