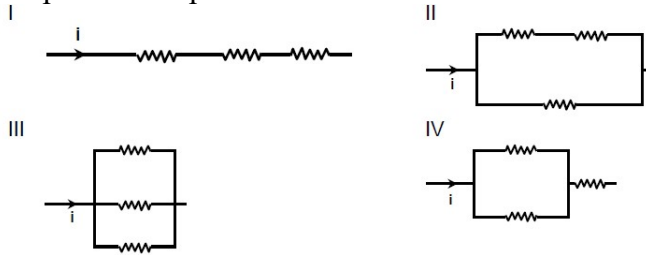


41. The three resistances of equal value are arranged in the different combinations shown below. Arrange them in increasing order of power dissipation



- (1) III < II < IV < I
- (2) II < III < IV < I
- (3) I < IV < III < II
- (4) I < III < II < IV

42. Masses of 3 wires of same metal are in the ratio 1 : 2 : 3 and their lengths are in the ratio 3 : 2 : 1. The electrical resistances are in ratio

- (1) 1 : 4 : 9
- (2) 9 : 4 : 1
- (3) 1 : 2 : 3
- (4) 27 : 6 : 1

43. Three resistances P, Q, R each of 2Ω and an unknown resistances S form the four arms of a Wheatstone's bridge circuit. When a resistance of 6Ω is connected in parallel to S, the bridge gets balanced. What is the value of S?

- (1) 2Ω
- (2) 3Ω
- (3) 6Ω
- (4) 1Ω

44. A 25W-220 V bulb and a 100W-220V bulb are joined in series and connected to the mains. Which bulb will glow brighter?

- (1) 25 W bulb
- (2) 100 W bulb
- (3) First 25 W bulb and then 100 W bulb
- (4) Both will glow with some brightness


45. The potential difference in open circuit for a cell is 2.2 volts. When a 4 ohm resistor is connected between its two electrodes the potential difference becomes 2 volts. The internal resistance of the cell will be

- (1) 1 ohm
- (2) 0.2 ohm
- (3) 2.5 ohm
- (4) 0.4 ohm

46. A potentiometer wire is 10 m long and has a resistance of 18Ω . It is connected to a battery of emf 5 V and internal resistance 2Ω . Calculate the potential gradient along the wire.

- (1) 0.65 Vm^{-1}
- (2) 0.45 Vm^{-1}
- (3) 0.35 Vm^{-1}
- (4) 0.25 Vm^{-1}

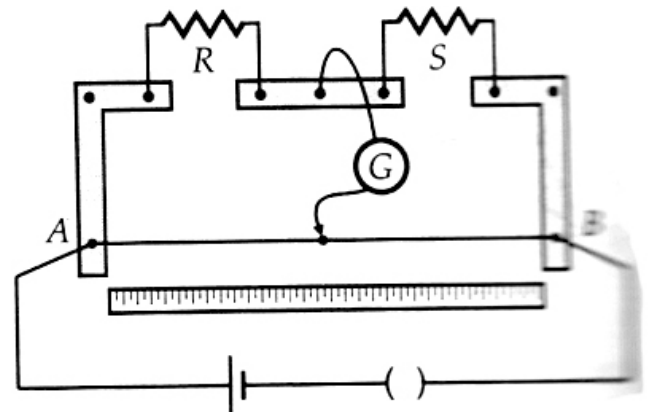47. In metre bridge, the null point is found at a distance of 60.0 cm from A. If now a resistance of 5Ω is connected in series with S, the null point occurs at 50 cm. Determine the values of R and S.




- (1) 25Ω
- (2) 15Ω
- (3) 35Ω
- (4) 45Ω

48. The emf of a cell is 1.5 V. On connecting a 14Ω resistance across the cell, the terminal p. d. falls to 1.4 V. Calculate the internal resistance of the cell


- (1) 4Ω
- (2) 3Ω
- (3) 2Ω
- (4) 1Ω

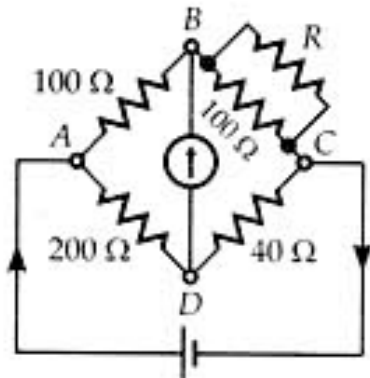49. The Wheatstone's bridge is showing no deflection in the galvanometer joined between the points B and D. The value of R is



- (1) 25Ω
- (2) 45Ω
- (3) 35Ω
- (4) 15Ω

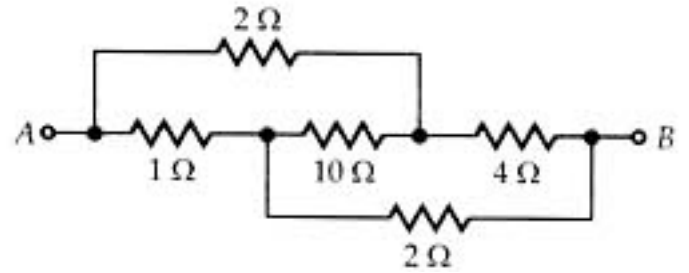50. Calculate the equivalent resistance between points A and B of the network shown in figure.



- (1) 2Ω
- (2) 4Ω
- (3) 1Ω
- (4) 3Ω